

Electricity and Magnetism — Lesson 3

ICSE Class 7 Physics · 10 MCQs · 1 mark each · Name: _____ Date: _____

Syllabus: Charges constituting current, circuit symbols & functions, series & parallel circuits, safety precautions before switching on.

Instructions: Each question has one correct option. Tick or circle the letter of the best answer. Attempt all questions.

1. An electric current is the flow of tiny charged particles called:

- A. photons
- B. electrons (charges)
- C. protons only
- D. atoms

2. Conventional current is taken to flow in the circuit from the ____ terminal of the cell.

- A. central
- B. negative
- C. earth
- D. positive

3. In a circuit diagram, a small circle with a cross inside stands for a:

- A. wire
- B. switch
- C. cell
- D. lamp (bulb)

4. A gap in a circuit diagram bridged by a movable lever represents a:

- A. cell
- B. switch
- C. resistor
- D. bulb

5. Components joined one after another in a single path are connected in:

- A. a short
- B. series
- C. a branch
- D. parallel

6. In a series circuit, the current through each component is:

- A. the same
- B. zero
- C. doubled
- D. different

7. In a parallel circuit, if one branch is switched off, the other branches:

- A. reverse
- B. burn out
- C. keep working
- D. also switch off

8. If removing one bulb from a string makes all the others go out, the bulbs were connected in:

- A. series
- B. a magnet
- C. parallel
- D. two circuits

9. Before switching on a newly made circuit, you should check that all connections are:

- A. tight and correct
- B. hot
- C. loose
- D. wet

10. The wires and terminals of a circuit are made of conductors so that they:

- A. stop the current
- B. store charge
- C. let the current pass easily
- D. insulate the circuit

Answer Key

1. B

2. D

3. D

4. B

5. B

6. A

7. C

8. A

9. A

10. C